

# Touchless Water Tap System (Arduino Project)

**BY-ABHINANDAN RAJ**

## Project Overview

The **Touchless Water Tap System** is an automatic water dispensing system that works **without touching the tap** 🙅‍♂️ 🚫.

When a hand is placed under the tap, water starts flowing automatically 💧.

When the hand is removed, the water stops.

This project improves **hygiene** and helps in **saving water** 🌍.

## Components Used

Component	Emoji	Purpose
Arduino UNO	🧠	Controls the entire system
Ultrasonic Sensor (HC-SR04)	📡	Detects hand movement
Relay Module (5V)	🔌	Switches the pump ON/OFF
DC Water Pump	💧	Pumps the water
External Battery / Power Adapter	🔋	Supplies power to the pump
Breadboard	🧱	For easy connections
Jumper Wires	🔌	Electrical connections
Water Pipe / Tube	🚰	Water outlet

## Component Connections

### Ultrasonic Sensor to Arduino

- **VCC** → 5V ⚡
- **GND** → GND
- **TRIG** → Digital Pin **9**
- **ECHO** → Digital Pin **10**

### Relay Module to Arduino

- **VCC** → 5V
- **GND** → GND
- **IN** → Digital Pin **8**

### Water Pump + Relay + Battery (Important ⚠)


❌ Do NOT connect the pump directly to Arduino or breadboard

Relay Terminal Connections:

- **COM** → One wire of the pump
- **NO (Normally Open)** → Battery **Negative (-)**
- **Other pump wire** → Battery **Positive (+)**

👉 When the relay turns ON, the circuit completes and the pump starts 💧

## Working Principle

- 1 The ultrasonic sensor continuously measures distance 
- 2 When a hand comes within **10–15 cm** 🖐

- 3 Arduino activates the relay 🧠 → ↺
- 4 Relay turns the water pump ON 💧
- 5 When the hand is removed
- 6 Arduino turns the relay OFF → pump stops 🚫

## Control Logic (Simple)

IF hand detected

→ Turn pump ON 💧

ELSE

→ Turn pump OFF 🚫

## Advantages

- 🧼 Touch-free operation (better hygiene)
- 💧 Saves water
- ⚡ Low power consumption
- 🧠 Fully automatic system
- 😊 Easy and safe to use

**BY-ABHINANDAN RAJ**